

Answer all the following questions

1) Find the area of the parallelogram that has the vectors $\underline{u}=(2, -1, 0)$ & $\underline{v}=-i+2j$ as two adjacent sides then find $\underline{w}$ the normal vector to both $\underline{u}$ and $\underline{v}$ and calculate the volume of the parallelepiped having $\underline{u}$, $\underline{v}$ and $\underline{w}$ as adjacent edges .

2) Find a set of parametric equations and symmetric equations of the line passes through the point $(-3, 5, 4)$ and is parallel to the line given by:

$$\frac{x-1}{3} = \frac{y+1}{-2} = z-3$$

3) In 3-D describe and sketch the graph of
i) $3x+4y+2z=12$
ii) $y=3$

4) In 3-D describe and sketch the graph of each of the following and describe the trace of each at XZ-plane:
i) $x^2-4z+3y^2+4z^2=12$
ii) $x^2-4z+3y^2-2x-4z^2=12-6y$

5) In 3-D describe and sketch $f(x,y) = x^2+8y^2$ and find the direction derivative of $f(x,y)$ at $(1, 0)$ in the direction of $\underline{v}=3i-4j$

6) For the curve represented by $\underline{r}(t) = 3t \ i + 2t^2 \ j$ find:
i) the unit tangent vector at $t=1$
ii) the principal unit normal vector at $t=2$
iii) the curvature and the value of the radius of curvature at $t=3$

7) For the hyperboloid surface given by the quadratic equation;
 $z^2-2x^2-2y^2=12$ find the equation of the tangent plane and the normal line at the point $(1, -1, 4)$

Best wishes Dr. M. Shehata (10 points)

السؤال الأول :
(أ) باستخدام قوانين الاتزان كيف تحصل على المعادلة العامة للغازات .

ب) 85 سم^3 من غاز CO_2 ينتشر خلال ثقب ثقوب ضيقة في 170 ثانية و 100 سم^3 من غاز NH_3 ينتشر خلال نفس الثقوب في 124.3 ثانية . احسب الوزن الجزيئي للغاز CO_2 علما بان الوزن الجزيئي للغاز النشادر هو 17 .

السؤال الثاني :
(أ) كيف يمكن قياس القوة الدافعة الكهربية لخلية ؟

ب) 0.0825 جرام من عينة غاز تشغل 27 سم^3 عند درجة حرارة 16.5 درجة وضغط 704 ملليمتر زئبق . احسب الوزن الجزيئي للغاز ($R=82.05$) .

السؤال الثالث :
(أ) اذكر الطرق المختلفة للوقاية من التآكل .

ب) اشرح خلية دانيال مع ذكر معادلات التفاعل بالتفصيل داخل الخلية .

السؤال الرابع :
(أ) اذكر بالتفصيل طرق صناعة الاسمنت .

(ت) اذكر بالتفصيل أنواع الاسمنت المختلفة .

مع التمنيات بالنجاح

1. Determine the current for each diode circuit in figure 1a, assume that the forward resistance for each silicon diode is 25Ω and the reverse leakage resistance is $100 \text{ M}\Omega$.

2. Determine the voltage with respect to ground at each point in fig. 1.b (the diodes are silicon)

3. Calculate I_C and V_{CE} for the circuit shown in figure 1c

4. Determine $I_{C(sat)}$ for the transistor in figure 2a. What is the value of I_B necessary to produce saturation? What minimum value of V_{IN} is necessary for saturation?

5. For the circuit shown in fig. 2b: Determine V_B and the Q-point values.

6. Which of the LEDs in figure 2c emit light, and which do not?

7. Draw the output voltage waveform V_{out} and determine the peak and the average output voltage of the circuit shown in figure 3a. What is the PIV for each diode?

8. Determine I_{FB} , I_C , I_E , β , V_{CE} , and $V_{CE(sat)}$ in the circuit shown in figure 3b. The transistor has a $\beta_{DC} = 200$

9. Determine the voltage waveform across R_L for each limiter circuit in figure 3c.

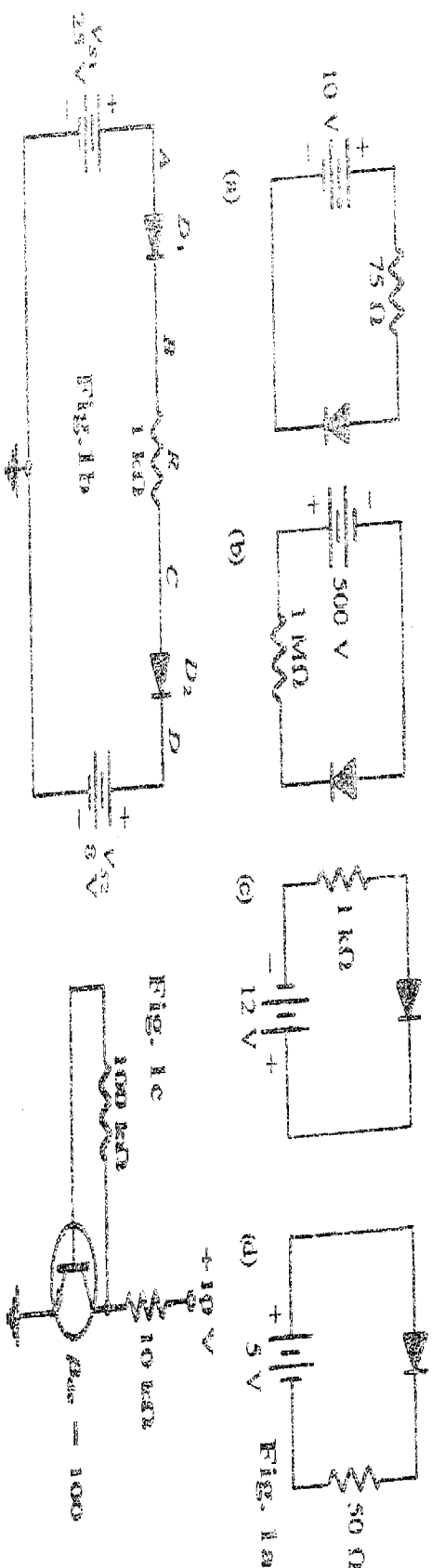


Figure 1

P.T.O

Beni-Suef University
Industrial Education College

Electrical Technology
Second Year
Examiner: Dr/Ala HASSAN

Topic: ACX1, ACX2, ACX3, ACX4

Final Exam
Date: 26/1/2010
Time: one hour

Q21(a) State Kirchhoff's laws.
Find the current and power supplied by the 24 volt source in the circuit shown in Fig.(1)
Use Delta-to-WYE transformation

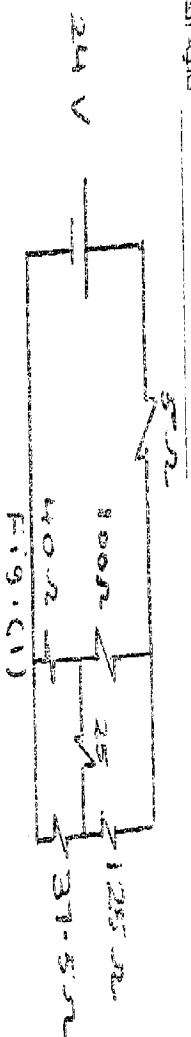


Fig. (1)

Q22) (a) In the Fig.(2) determine the nodes, essential nodes, branches, essential branches and meshes.
(b) use mesh to find the currents in all branches in the circuit in Fig.(2) given that $E_1 = 5$ A, $R_1 = 20 \Omega$, $R_2 = 10 \Omega$, $R_3 = 40 \Omega$, $R_4 = 15 \Omega$



Fig. (2)

$E_1 = 100$ volt

Q3) Two batteries A and B are connected across their terminals, A has an e.m.f of 12 volt and internal resistance of 2Ω ; B has an e.m.f of 8 volt and internal resistance of 1Ω . Use Kirchhoff's laws to determine the values and directions of the currents flowing in each of the batteries and in the external resistance. Also determine the potential difference across the external resistance

Q4) (a) A sinusoidal voltage is given by the expression $V(t) = 300 \cos(120\pi t + 30^\circ)$ what is the:- period of the voltage in ms- frequency in Hz- magnitude of v at $t = 2.778$ ms.
(b) In Fig.(3) find the resistance between A and B also determine the current in each resistance

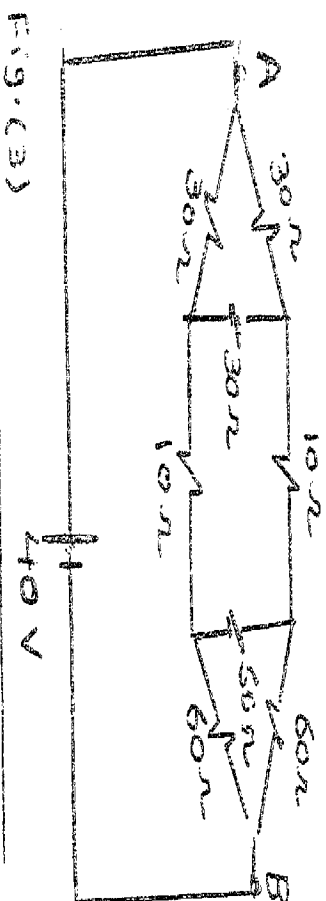


Fig. (3)


قسم العلوم الأساسية
مادة : فيزياء
الفرقة الثانية (الكهرباء والالكترونيات) (تحكم)

جامعة بني سويف
كلية التعليم الصناعي
الزمن : ثلاث ساعات

امتحان نهائية الفصل الدراسي الأول ٢٠٠٤ / ٢٠٠٥


اجب عن الاسئلة التالية:
الاسئلة الأولى: (١٠ درجات)

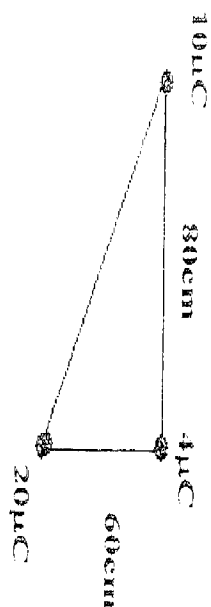- (١) عرف قانون كولوم مع كتابة الصيغة الرياضية للقانون.
- (ب) اوجد قيمة واتجاه القوة الكهربائية المؤثرة على الشحنة $20 \mu C$ في الشكل المقابل.



(السمي إلى الثانية: ١٥ درجة)

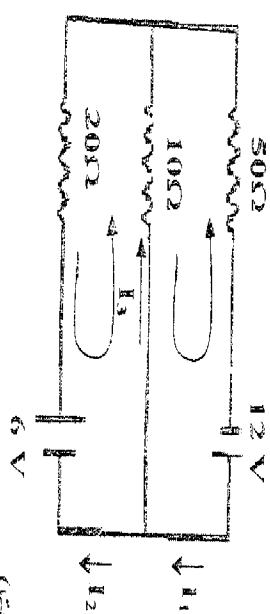- (١) اثبت ان المقاومة الكهربائية لموصل تعتمد على الأبعاد الهندسية لهذا الموصل.
- (ب) باستخدام قانون كيرشوف الثاني اوجد التيار الكهربى و فرق الجهد عبر كل مقاومة في الشكل التالي:



(السمي إلى الثالثة: ١٠ درجات)

- (١) باستخدام قانون جاوس اوجد شدة المجال الكهربى الناشئ عن سلك طويل مشحون.
- (ب) صفحتين متوازيتين ومتوازيتين فإذا كانت الكثافة السطحية للشحنة على الصفيحة الأولى هي $+2 \lambda$ وعلى الصفيحة الأخرى -2λ . اوجد قيمة المجال الكهربى عند النقط التالية:
- (١) على يسار اللوحين (٢) بين اللوحين (٣) على يمين اللوحين

(السؤال الرابع: ١٠ درجات)

- (١) اثبت ان فرق الجهد الكهربى بين نقطتين A و B و اللتان تبعدان مسافة rA و rB يعطى بالعلاقة:

$$V_B - V_A = \frac{q}{4\pi\epsilon_0} \left(\frac{1}{r_B} - \frac{1}{r_A} \right)$$

الكل خاتمة

السؤال الأول :

- أ) باستخدام قوانين الغازات كيف تحصل على المعادلة العامة للغازات.
ب) اشرح كيف تتم عملية التقطير التجزيئي لسائلين تاما الامتزاج.

السؤال الثاني:

- أ) اشرح قاعدة الطور. ثم اذكر الانواع الأساسية من منحنيات الأطوار مع تطبيق قاعدة الطور في كل نوع.

- ب) اشرح مع الرسم منحنيات درجة الذوبان للحالات المختلفة للسوائل محددة الامتزاج.

السؤال الثالث:

- أ) عرف تاكل المعادن مع ذكر الأضرار الصناعية للتاكل والطرق المختلفة للوقاية من التاكل.

- ب) اذكر أنواع الطوب. مع ذكر بالتفصيل خطوات صناعة الطوب الأحمر والطوب الرمل.

السؤال الرابع:

- أ) اذكر بالتفصيل طرق صناعة الأسمنت .

- ب) اذكر بالتفصيل أنواع الأسمنت المختلفة.

السؤال الخامس:

- أ) اذكر بالتفصيل مراحل صناعة الزجاج. مع ذكر الأنواع المختلفة للزجاج مع توضيح الفرق في كل نوع.

- ب) اشرح كيف يحدث التاكل مع ذكر الحالات المختلفة التي يحدث عندها التاكل مع ذكر مثال لكل نوع (مع الرسم).



Faculty of Industrial Education
All Departments
End of 1st Term Exam – January 2009/2010
English, 2nd Year

Read the following passage and then answer the questions below:

Civil engineering is a professional engineering discipline that deals with the design, construction and maintenance of the physical and naturally built environment, including works such as bridges, roads, canals, dams and buildings. Civil engineering is the oldest engineering discipline after military engineering, and it was defined to distinguish nonmilitary engineering from military engineering. It is traditionally broken into several sub-disciplines including environmental engineering, geotechnical engineering, municipal or urban engineering, coastal engineering, surveying, and construction engineering.

- 1- What does civil engineering deal with?
- 2- What is civil engineering called so?
- 3- What are the branches of civil engineering?
- 4- What is the opposite of Civil Engineering?
- 5- Summarize the passage to three sentences.

السؤال الأول: أ) اذكر مع الشرح الخواص المختلفة للكتان واستعملاته.

ب) اشرح بالتفصيل الخواص المحددة لجودة القطن.

السؤال الثاني: أ) اذكر مع الشرح العوامل المؤثرة على رتبة القطن

ب) ما هي أنواع الصوف ؟ اذكر مع الشرح الشوائب الموجودة بالصوف الخام.

السؤال الثالث: أ) اشرح العوامل التي تحدد الرتبة في الصوف الخام.

ب) ما هي عملية تليد الصوف؟

السؤال الرابع: أ) وضح طرق التبييض المختلفة للألياف القطنية

ب) اذكر بالتفصيل أنظمة تقسيم الصبغات . مع ذكر أمثلة لكل نوع.

مع التلميحات بالنجاح

- ١- اذكر مواضع همز الوصل ، مع ذكر الأمثلة و الشواهد .
 - ٢- وضع حكم الفعل الذي تحته خط من حيث الإعراب
 - لن يفتح الكسول
 - لم يفتح الرجل في العمل
 - إن يذاكر الطالب ينجح
 - يذاكر الطالب دروسه بجد
 - ٣- اختر الإجابة الصحيحة:
 - ما أحسن زيدا
 - ما أحسن ربة
 - ما أحسن زيد
 - ما أحسن زيد
- السؤال الثاني
- ١- ذهبت في رحلة لمدة (٢ أسبوع) ، وكنا (١٥ طالب) وزرنا (٥ موقع سياحية) حول الأرقام
 - إلى حروف ، و اكتب المعاني الصحيحة
 - ٢- اذكر ثلاثة من مواضع كسر همزة إن وجوبا .
 - ٣- اختر الإجابة الصحيحة :
 - الضبط الصحيح لكلمة المناخ (المناخ) - المناخ
 - الرجل متضلع (من - في) - الصنعة
 - هذا فعل (ماضي - ماض)
 - ٤- اذكر مواضع استخدام الفصلة المنقوطة (؛) مع ذكر الأمثلة على ذلك

أجبت عن سؤال واحد فقط سائلك :

قال الشاعر : جريت صدم من فوم لجاهر منقول :- وصر منقاري من جوى البنية في شمل
١- اذكر المناهج المستخدمة في كتابة نصيحتي القصيدة
٢- حلل المصنف من حيث الشكل والمضمون
٣- استخرج ثلاث صور بلاغية من النصائح الخمسة المذكورة وعرّفها .
السؤال الثاني :

- ١- صحح صديقي بياض نجيب :- بضم صديقه وفتح بياضه وفتح نجيب
- ٢- أكتب أربعين بيتا بعد هذا البيت
- ٣- حلل المقامات التي سكتها بيت من حيث المضمون
- ٤- اذكر عناصري بناء هذه المقامة
- ٥- وضع لي بيت آخر من المقامات المرسية في الترتاب الأدبي


قسم المعلومات الأساسية
مادة : فيزياء ٢
الفرقة الثانية (الاجهزة + مدني)

جامعة بني سويف
كلية التعليم الصناعي
الزمن : ثلاث ساعات

امتحانات نهائية الفصل الدراسي الأول ٢٠٢٠/٢٠١٩

اجب عن الاسئلة التالية:

المسألة الأولى: (١٠ درجات)

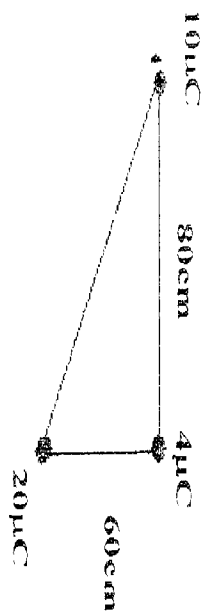


(١) عرف قانون كولوم مع كتابة الصيغة الرياضية للقانون
(ب) اوجد قيمة واتجاه القوة الكهربائية المؤثرة على الشحنة
20nC في الشكل المقابل

المسألة الثانية: (١٥ درجة)

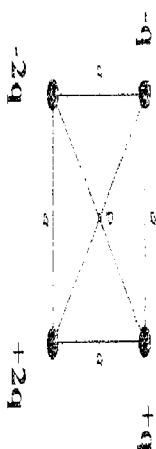(١) اذكر خصائص خطوط المجال الكهربائي

(ب) اوجد قيمة واتجاه المجال الكهربائي عند النقطة P في الشكل التالي علما بان $a=10\text{cm}$ و $q=10^{-6}\text{C}$



المسألة الثالثة: (١٠ درجات)

(١) باستخدام قانون جاوس اوجد شدة المجال الكهربائي الناشئ عن سلك طويل مشحون

(ب) صفيحتين متوازيتين ومتوازيتين فإذا كانت الكثافة السطحية للشحنة على الصفيحة الاولى هي $+2\lambda$ وعلى الصفيحة الاخرى -2λ . اوجد قيمة المجال الكهربائي عند النقط التالية:

(١) على يسار اللوحين (٢) بين اللوحين (٣) على يمين اللوحين

المسألة الرابعة: (١٠ درجات)

(١) اثبت ان فرق الجهد الكهربائي بين نقطتين A و B و اللتان تبعدان مسافة rA و rB يسطى بالمعادلة:

$$V_B - V_A = \frac{q}{4\pi\epsilon_0} \left(\frac{1}{r_B} - \frac{1}{r_A} \right)$$


انظر حلقة

قسم المطبق الاماسية
مادة : فيزياء
الفرقة الثانية (الكتر وزيات +تحكم)

جامعة بني سويف
كلية التعليم الصناعي
الزمن : ثلاث ساعات


امتحان نهائية الفصل الدراسي الأول ٢٠٠١/٢٠٠٢

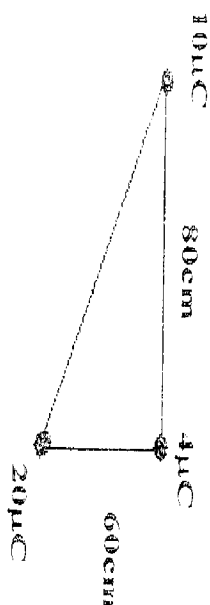اجب عن الاسئلة التالية:
السؤال الاول : (١٠ درجات)



- (١) عرف قانون كولوم مع كتابة الصيغة الرياضية للقانون.
(ب) اوجد قيمة واتجاه القوة الكهربائية المؤثرة على الشحنة 20μC في الشكل المقابل.

السؤال الثاني : (١٥ درجة)

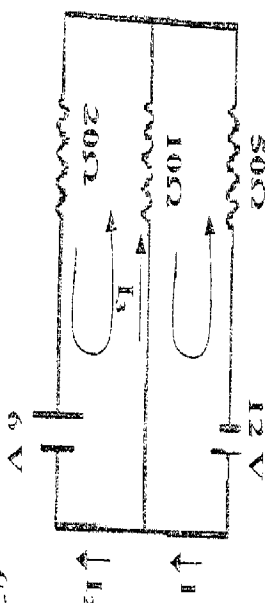

- (١) اثبت ان المقاومة الكهربائية لموصل تعتمد على الانواع الهندسية لهذا الموصل.
(ب) باستخدام قانون كيرشوف الثاني اوجد التيار الكهربى و فرق الجهد عبر كل مقاومة في الشكل التالي :

السؤال الثالث : (١٠ درجات)

- (١) باستخدم قانون جاوس اوجد شدة المجال الكهربى الناشى عن سلك بطول مشهور.
(ب) صفحتين معدنيتين ومتوازيتين فإذا كانت الكثافة السطحية للشحنة على الصفيحة الاولى هي $+2\lambda$ وعلى الصفيحة الاخرى -2λ . اوجد قيمة المجال الكهربى عند النقط التالية :

(١) على يسار اللوحين (٢) بين اللوحين (٣) على يمين اللوحين

- (١) اثبت ان فرق الجهد الكهربى بين نقطتين A و B و اللتان تبعدان مسافة rA و rB يعطى بالعلاقة :

$$\therefore V_B - V_A = \frac{q}{4\pi\epsilon_0} \left(\frac{1}{r_B} - \frac{1}{r_A} \right)$$

انذار خاتمة

1. a-Determine the current for each diode circuit in figure 1a, assume that the forward resistance for each silicon diode is 25Ω and the reverse leakage resistance is $1000 \text{ M}\Omega$.
- b-Determine the voltage with respect to ground at each point in fig. 1.b (the diodes are silicon)
- c-Calculate I_C and V_{CE} for the circuit shown in figure 1c

2. a-Determine $I_{C(sat)}$ for the transistor in figure 2a. What is the value of I_B necessary to produce saturation? What minimum value of V_{in} is necessary for saturation?
- b-For the circuit shown in fig.2b: Determine I_B and the Q-point values
- c-Whether of the LEDs in figure 2c emit light, and which do not?
3. a-Draw the output voltage waveform V_{out} and determine the peak and the average output voltage of the circuit shown in figure 3.a What is the PIV for each diode
- b-Determine I_B , I_C , I_E , α , V_{CE} , and V_{CEB} , in the circuit shown in figure 3b. The transistor has a $\beta_{DC} = 200$
- c-Determine the voltage waveform across R_L for each limiter circuit in Figure 3c.

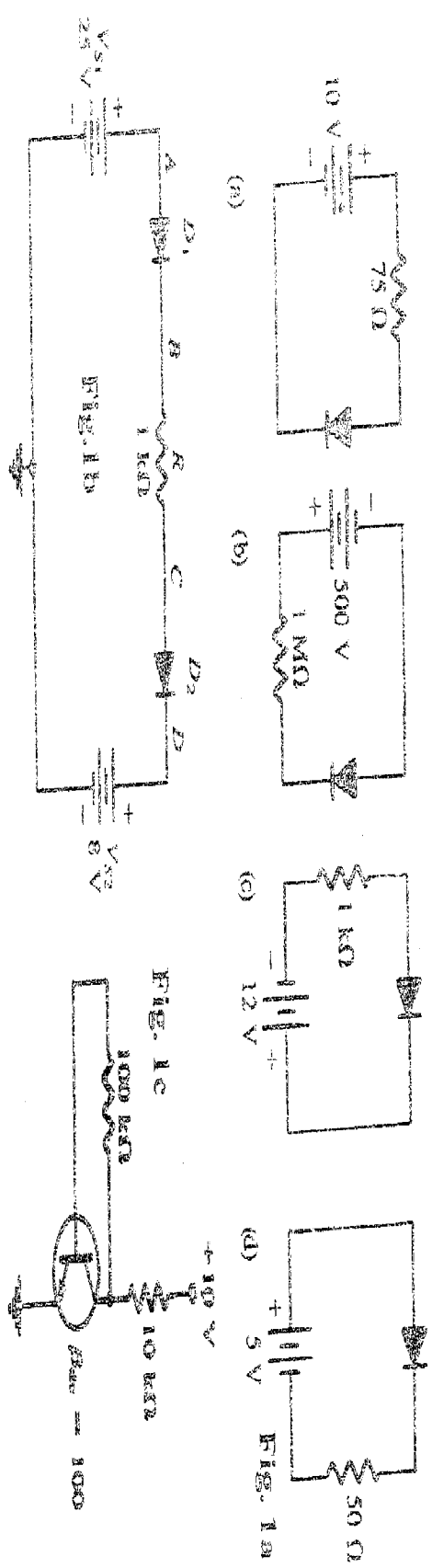


FIGURE 1

P.T.O

Beeth-Suof University
Industrial Education College

Electrical Technology
Second Year

Examiner: Dr. ALI HASSAN

Asses: Ahmed - 25.3 and 35.50


Final Exam

Date: 26/1/2010

Time: one hour

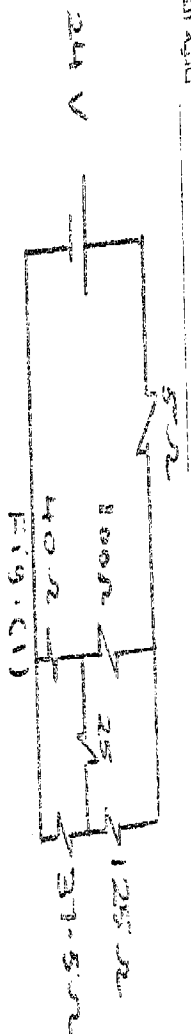Q21(a) Solve Kirchhoff's laws.


Find the current and power supplied by the 24 volt source in the circuit shown in Fig.(1) Use Delta-to-WYE transformation



Q21 (a) in the Fig.(2) determine the nodes, essential nodes, branches, essential branches and meshes.

(b) use mesh to find the currents in all branches in the circuit in Fig.(2) given that $R_1 = 5 \Omega$, $R_2 = 20 \Omega$, $R_3 = 10 \Omega$, $R_4 = 40 \Omega$, $R_5 = 15 \Omega$


$E_1 = 100$ volt

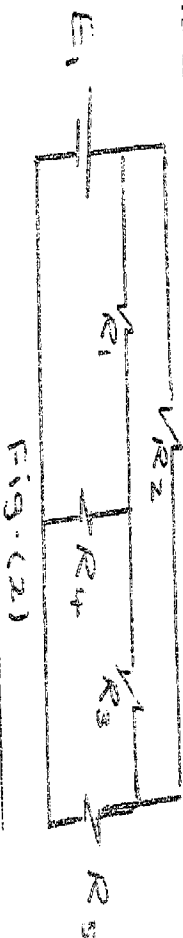

Q31 Two batteries A and B are connected across their terminals. A has an e.m.f of 12 volt and internal resistance of 2Ω . B has an e.m.f of 8 volt and internal resistance of 1Ω . Use Kirchhoff's laws to determine the values and directions of the currents flowing in each of the batteries and in the external resistance. Also determine the potential difference across the external resistance

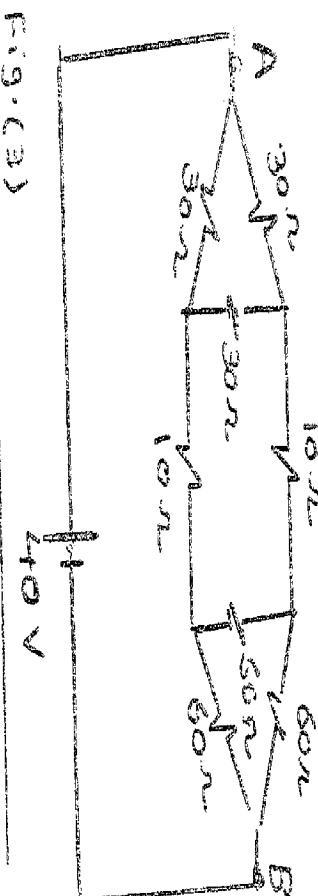
Q41 (a) A sinusoidal voltage is given by the expression $V(t) = 300 \cos(120\pi t + 30^\circ)$. What is the:- period of the voltage in ms-

frequency in Hz - magnitude of v at $t = 2.78$ ms.
(b) in fig.(3) find the resistance between A and B also determine the current in each resistance



The elevation and end elevation of a bracket are shown. Draw, full size the following: -

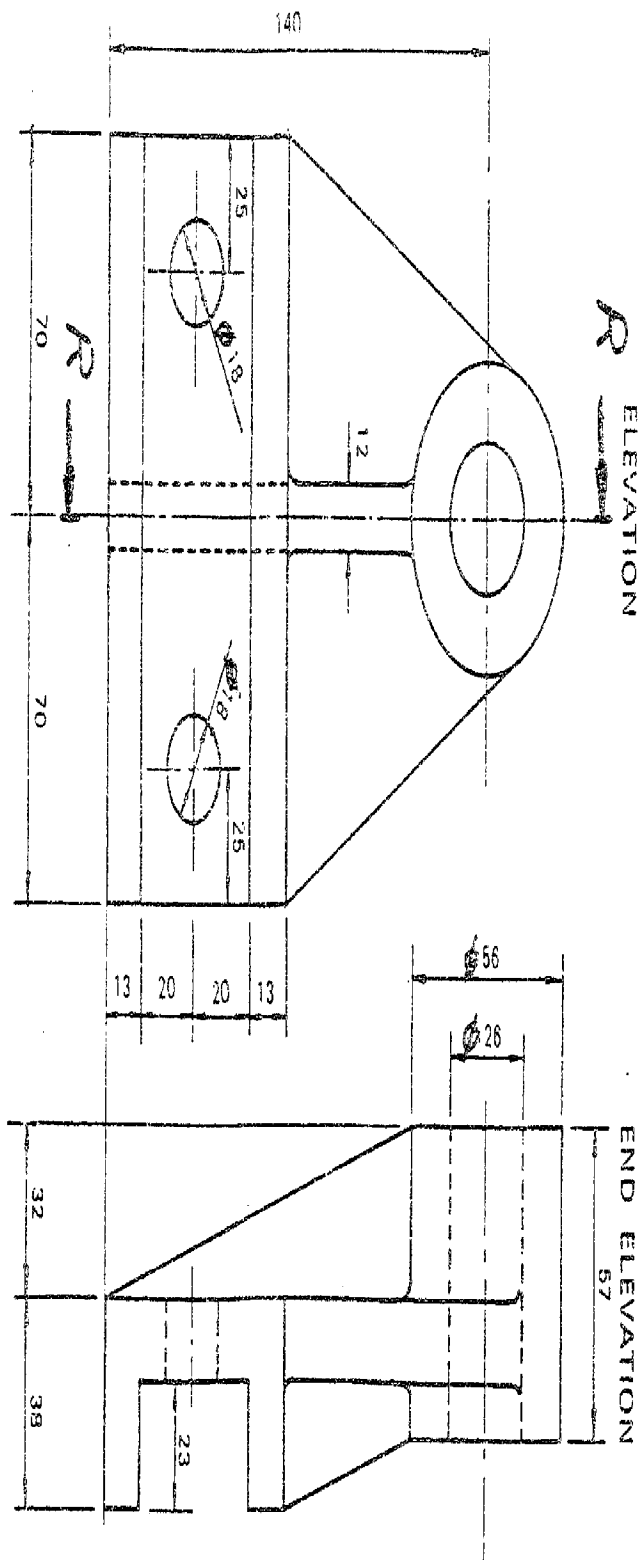1. The given elevation.
2. The sectional end elevation on R-R.
3. The Plan.
4. Enter all dimensions on your drawings.



Find the current and power supplied by the 2-Volt source in the circuit shown in Fig. 1)

[illegible]


1031 Two batteries A and B are connected across their terminals. A has an e.m.f. of 12 volt and internal resistance of 2Ω; B has an e.m.f. of 8 volt and internal resistance of 1 Ω. Use Kirchhoff's laws to determine the values and directions of the currents flowing in each of the batteries and in the external resistance. Also determine the potential difference across the external resistance.

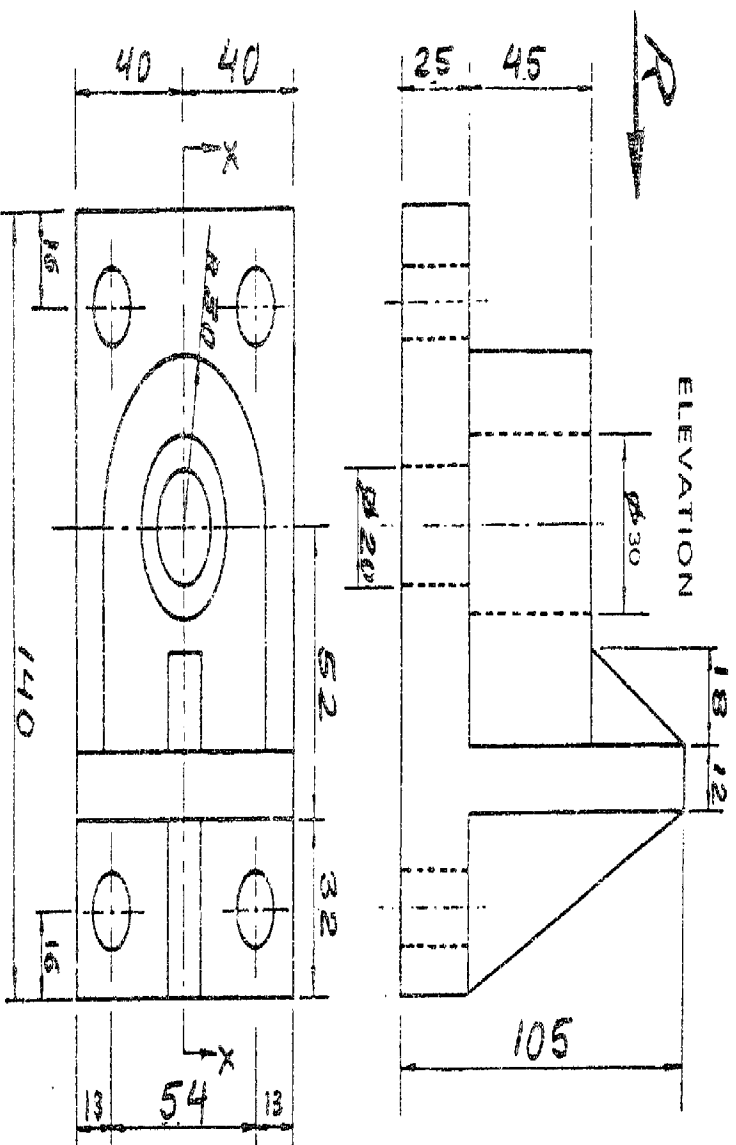Q41 (a) A sinusoidal voltage is given by the expression $v(t) = 300 \cos(120\pi t + 30^\circ)$. What is the:— period of the voltage in ms— frequency in Hz— magnitude of v at $t = 2.778$ ms— (b) In fig. (3) find the resistance between A and B also determine the current in each resistance



The elevation and plan of a cast iron bearing are shown. Draw, full size the following:-

- 1- The given plan.
- 2- Sectional elevation on X-X.
- 3- End elevation looking in the direction of arrow R.
- 4- Enter all dimensions on your drawings.



THICKNESS OF WEBS: 12 MILLIMETRES
BOLT HOLES IN BASE: 12 MILLIMETRES
DIAMETER

جامعة بني سويف
كلية التعليم الصناعي
امتحان الفصل الدراسي الأول للعام : ٢٠٠٩
الفرقة الثانية :
أجب عن الأسئلة التالية:
السؤال الأول

المادة : اللغة العربية

امتحان الفصل الدراسي الأول للعام : ٢٠٠٩

الفرقة الثانية :
أجب عن الأسئلة التالية:

السؤال الأول

١- اذكر موضحا من تأصيل هذه الأمثلة والثوابد .
٢- وضع حكم العمل الذي نعت به خط من حيث الإعراب

٣- لن يفتح الكسول

٤- لم يفتح الرجل في العمل

٥- إن يذاكر الطالب يفتح

٦- يذاكر الطالب دروسه بعد

٧- اختر الإجابة الصحيحة:

٨- ما أحسن زينة

٩- ما أحسن زينة

١٠- ما أحسن زينة

١١- ما أحسن زينة

١٢- ما أحسن زينة

١٣- ما أحسن زينة

١٤- ما أحسن زينة

١٥- ما أحسن زينة

١٦- ما أحسن زينة

١٧- ما أحسن زينة

١٨- ما أحسن زينة

١٩- ما أحسن زينة

٢٠- ما أحسن زينة

٢١- ما أحسن زينة

٢٢- ما أحسن زينة

٢٣- ما أحسن زينة

٢٤- ما أحسن زينة

٢٥- ما أحسن زينة

٢٦- ما أحسن زينة

٢٧- ما أحسن زينة

٢٨- ما أحسن زينة

٢٩- ما أحسن زينة

٣٠- ما أحسن زينة

٣١- ما أحسن زينة

٣٢- ما أحسن زينة

٣٣- ما أحسن زينة

٣٤- ما أحسن زينة

٣٥- ما أحسن زينة

٣٦- ما أحسن زينة

٣٧- ما أحسن زينة

٣٨- ما أحسن زينة

٣٩- ما أحسن زينة

٤٠- ما أحسن زينة

٤١- ما أحسن زينة

٤٢- ما أحسن زينة

٤٣- ما أحسن زينة

٤٤- ما أحسن زينة

٤٥- ما أحسن زينة

٤٦- ما أحسن زينة

٤٧- ما أحسن زينة

٤٨- ما أحسن زينة

٤٩- ما أحسن زينة

٥٠- ما أحسن زينة

أجبت عن سؤال واحد فقط من بين:

السؤال الأول:

١- اذكر المناهج التي تليها في الأقسام

٢- حلل المرسية من حيث الشكل والمضمون

٣- استخرج ثلاث من البيانات الخمسة المذكورة ووضحها

٤- اشرح الهمزة

٥- اكتب أربعاً أبيات بعد هذا البيت

٦- حلل المقامات التي سكتها في البيت

٧- اذكر عناوينها في المقامات

٨- وضع لبيت آخر في المقامات المرسية في الأقسام

٩- اكتب أربعاً أبيات بعد هذا البيت

١٠- حلل المقامات التي سكتها في البيت

١١- اذكر عناوينها في المقامات

١٢- وضع لبيت آخر في المقامات المرسية في الأقسام

١٣- اكتب أربعاً أبيات بعد هذا البيت

١٤- حلل المقامات التي سكتها في البيت


١٥- اذكر عناوينها في المقامات

١٦- وضع لبيت آخر في المقامات المرسية في الأقسام


Final Term Exam. 2009 – 2010

Attempt all questions

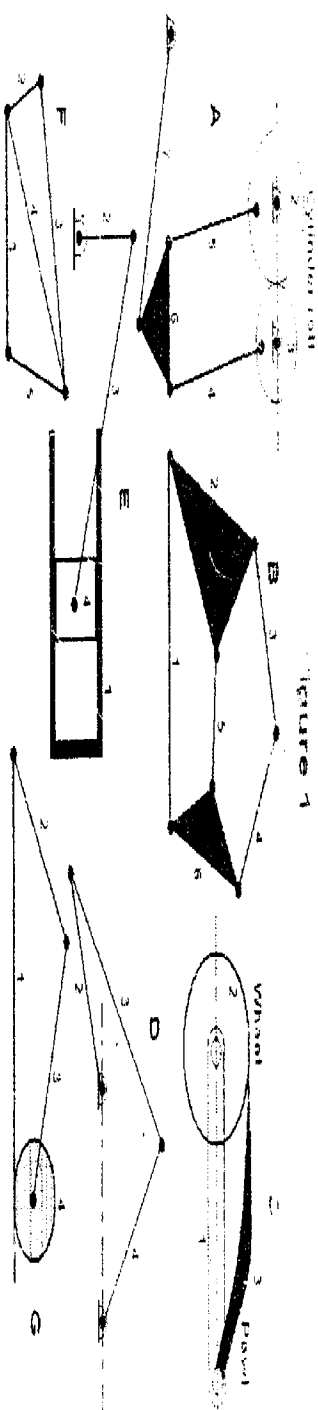1. Find the mobility of the following mechanisms shown in Figure (1) and also describe its type of motion.



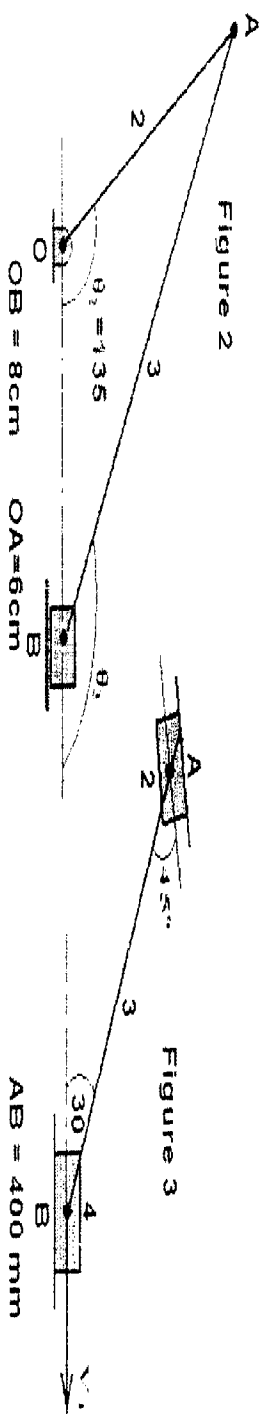2. Describe the motion of a particle P whose position changes with time according to the following equations: $x = 2 \cos 2\pi t$, $y = 2 \sin 2\pi t$, $z = 0$
3. Make a position analysis of the slider-crank mechanism shown in Figure (2). Determine the magnitude of AB and the angle θ_3 by using: – graphic approach – analytic approach – vector algebraic approach.



4. The velocity of point B of the linkage shown in Figure (3) is 40 m/sec. Find the velocity of point A and the angular velocity of link 3.

5. The angular velocity of link 2 of the drag-link mechanism shown in figure (4) is 16 rad/sec (ccw). Find the angular velocity of links 3 and 4 by using:– graphic approach – algebraic approach. Calculate the percentage of error between the two methods.

